


Ex

In the ckt,

$$V_1 = 3V_2$$

and V_1 and V_2 are in quadrature.

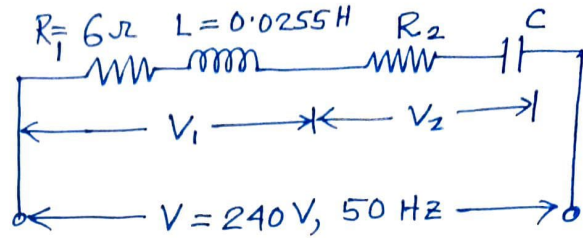Find R_2 and C . Also draw the phasor diagram.



Solⁿ. $X_L = 2\pi fL = 2\pi \times 50 \times 0.0255 = 8 \Omega$ (inductive reactance)


\bar{V}_1 and \bar{V}_2 are in quadrature and $\bar{V}_1 + \bar{V}_2 = \bar{V}$

$$\therefore V_1^2 + V_2^2 = V^2$$

$$\Rightarrow (3V_2)^2 + V_2^2 = (240)^2$$

$$\Rightarrow V_2 = 75.9 \text{ V} \quad \text{and} \quad V_1 = 3V_2 = 227.7 \text{ V}$$

The ckt can also be drawn as shown

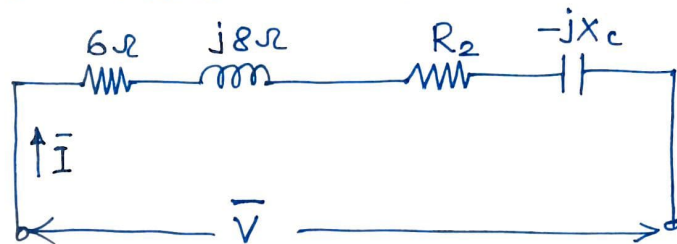

Taking \bar{I} as reference phasor, the phasor diagram is drawn.

$$\tan \theta_1 = \frac{8I}{6I} \Rightarrow \theta_1 = 53.1^\circ$$

$$\tan \theta_2 = \frac{IX_c}{IR_2} = \frac{X_c}{R_2}$$

$$\text{But } \theta_1 + \theta_2 = 90^\circ$$

[$\because V_1$ and V_2 in quadrature]

$$\theta_2 = 90^\circ - 53.1^\circ = 36.9^\circ$$

$$\text{Again } (6I)^2 + (8I)^2 = (227.7)^2 \Rightarrow I = 22.8 \text{ A (upper } \Delta)$$


$$\frac{X_c}{R_2} = \tan 36.9^\circ = 0.75 \Rightarrow X_c = 0.75 R_2$$

$$(IR_2)^2 + (IX_c)^2 = (75.9)^2 \quad (\text{lower } \Delta)$$

$$\Rightarrow R_2 = 2.664 \Omega \quad \text{and} \quad X_c = 0.75 \times 2.664 = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$\Rightarrow C = 1.594 \text{ mF}$$

(ii)

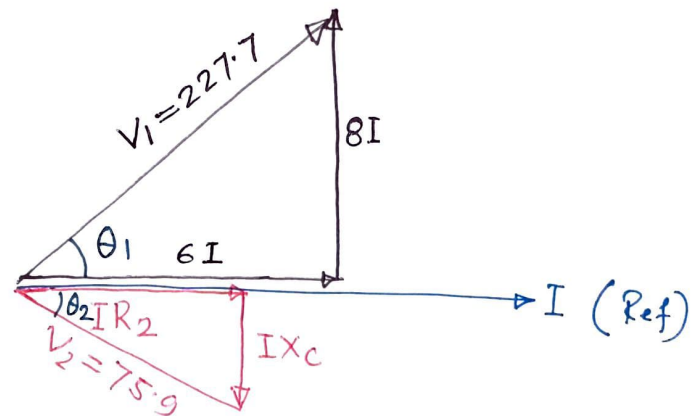


Ex

$$|\bar{I}| = 15 \text{ A}$$

Calculate (i) \bar{I}_1 (ii) \bar{I}_2

(iii) \bar{V}

Draw the phasor diagram.

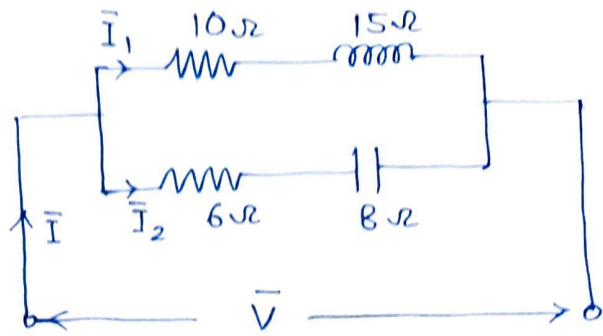

Soln. $\bar{Z}_1 = 10 + j15$, $\bar{Z}_2 = 6 - j8$


Assume that $\bar{I} = I \angle 0^\circ = 15 \angle 0^\circ$ (current is ref. phasor)

$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

According to current divⁿ method

$$\bar{I}_1 = \frac{\bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} \times \bar{I}$$
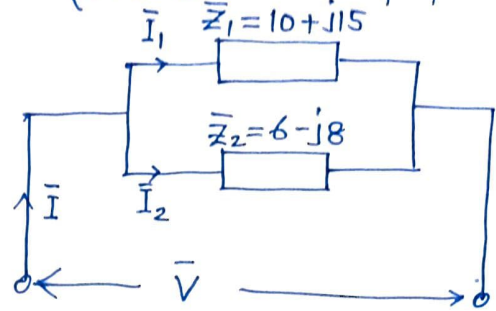
$$\bar{I}_2 = \frac{\bar{Z}_1}{\bar{Z}_1 + \bar{Z}_2} \times \bar{I}$$



$$\therefore \bar{I}_1 = \frac{6 - j8}{10 + j15 + 6 - j8} \times 15 \angle 0^\circ = 8.59 \angle -76.7^\circ \text{ A}$$


$$\text{ly, } \bar{I}_2 = 15.49 \angle 32.7^\circ$$

And $\bar{V} = \bar{I}_1 \bar{Z}_1 = \bar{I}_2 \bar{Z}_2$

$$= (8.59 \angle -76.7^\circ)(10 + j15)$$

$$= (8.59 \angle -76.7^\circ)(18.03 \angle 56.3^\circ)$$

$$= 154.9 \angle -20.4^\circ \text{ V}$$

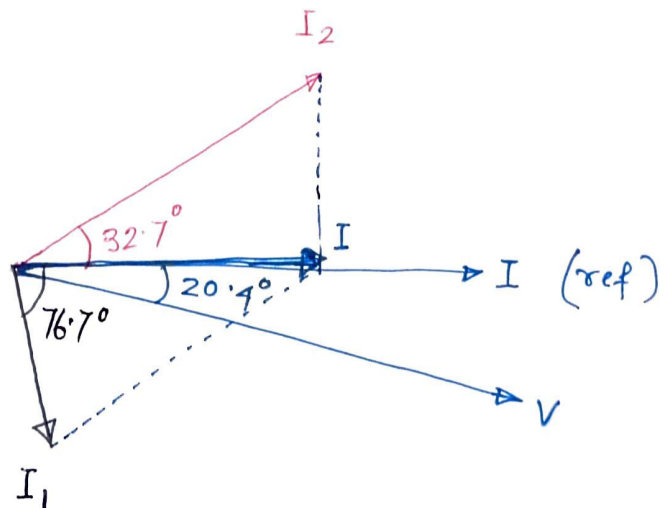


Ex. In the cut find

(i) \bar{I} if $\bar{I}_R = 0.02 \angle 30^\circ \text{ A}$

(ii) \bar{I}_R if $\bar{I} = 2 \angle -40^\circ \text{ A}$

(iii) Applied voltage

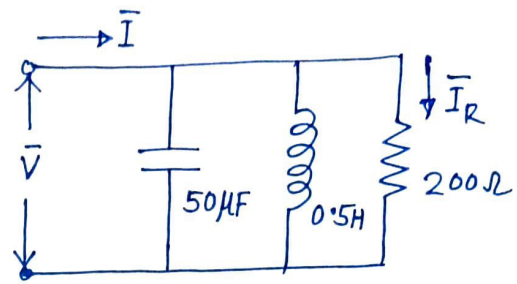


Also draw phasor diagram.

[Ans. $\bar{I} = 0.02 \angle 30^\circ \text{ A}$, $\bar{I}_R = 2 \angle -40^\circ \text{ A}$, $\bar{V} = 400 \angle -40^\circ \text{ V}$]

Ex. In the above cut find admittance, \bar{Y}_T (equivalent), $\bar{Y}_1, \bar{Y}_2, \bar{Y}_3$ and solve the above problem.

Ex. Compute the equivalent impedance \bar{Z}_{eq} and admittance \bar{Y}_{eq} for the four branch cut.

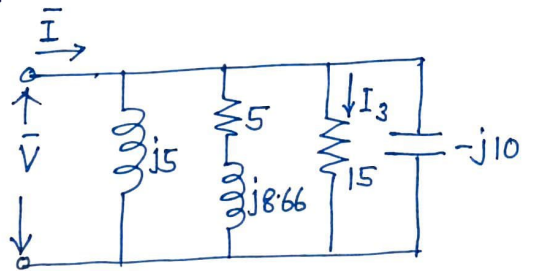
[Ans. $\bar{Z}_{eq} = 4.53 \angle 58.0^\circ$
 $\bar{Y}_{eq} = 0.221 \angle -58.0^\circ$]



If the total current I entering the cut is $33 \angle -13^\circ$ find branch current \bar{I}_3 and voltage \bar{V} .

[Ans. $\bar{V} = 149.5 \angle 45^\circ \text{ V}$, $\bar{I}_3 = 9.97 \angle 45^\circ \text{ A}$]

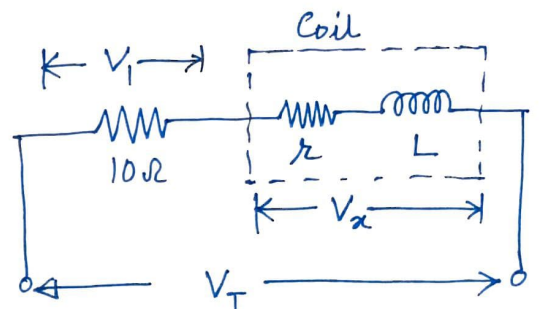Ex. In the given cut we have measured V_1, V_T and V_x using a voltmeter
 $V_1 = 20 \text{ V}$, $V_T = 36 \text{ V}$, $V_x = 22.4 \text{ V}$
 Find r and L .



[Ans. $r = 4.92 \Omega$, $L = 26.7 \text{ mH}$]


Power in sinusoidal steady state

A single-phase AC source supplying a load of impedance $Z < \theta$

Let $v(t) = \sqrt{2} V \sin \omega t \Rightarrow \bar{V} = V < 0^\circ$

$i(t) = \sqrt{2} I \sin(\omega t - \theta) \Rightarrow \bar{I} = I < -\theta$

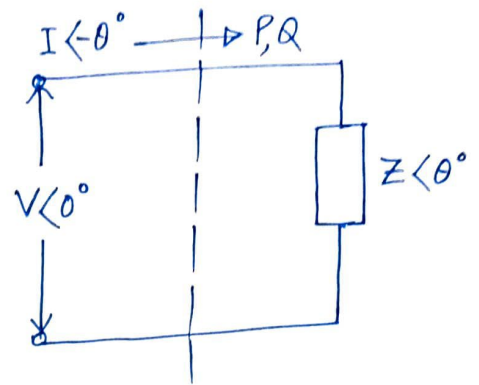$\bar{Z} = Z < \theta \quad \bar{I} = \frac{\bar{V}}{\bar{Z}}$




The instantaneous power delivered to the load is given by

$$\begin{aligned} p(t) &= v(t) i(t) = 2VI \sin \omega t \cdot \sin(\omega t - \theta) \\ &= VI (2 \sin \omega t \cdot \sin(\omega t - \theta)) \\ &= VI (\cos \theta - \cos(2\omega t - \theta)) \\ &= VI \cos \theta - VI \cos(2\omega t - \theta) \end{aligned}$$

\therefore Average power,
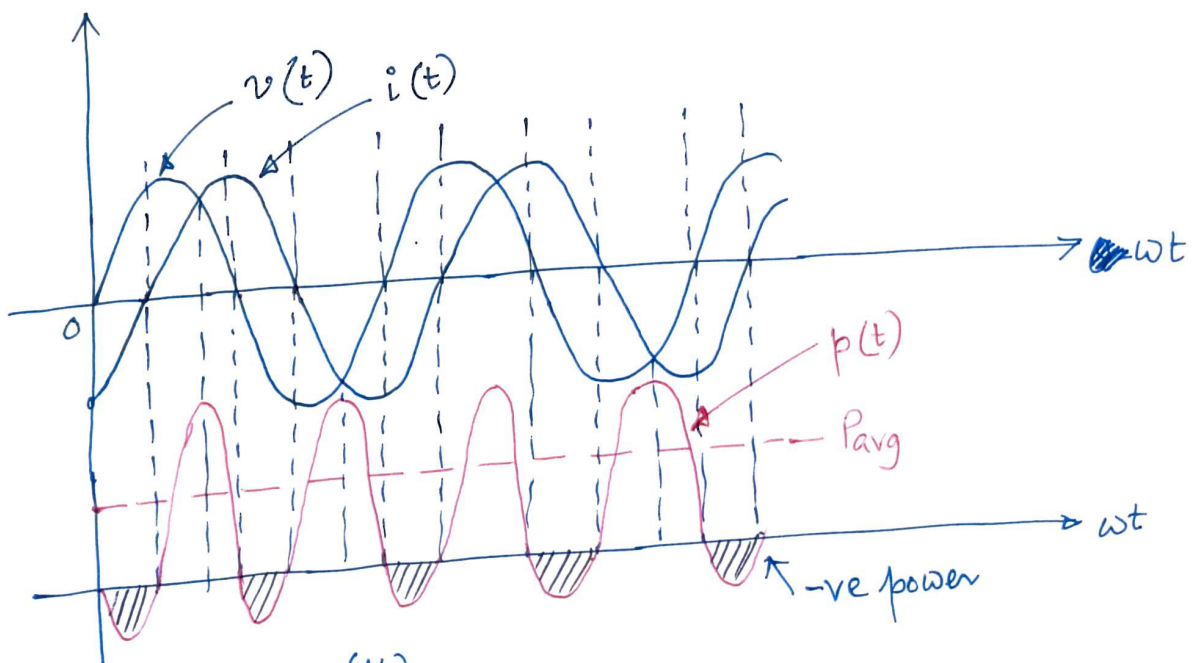
$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T [VI \cos \theta - VI \cos(2\omega t - \theta)] dt \\ &= \frac{1}{T} \int_0^T VI \cos \theta dt - \frac{1}{T} \int_0^T VI \cos(2\omega t - \theta) dt \\ &= VI \cos \theta - 0 \\ &= VI \cos \theta \end{aligned}$$



From equation

$$p(t) = VI \cos \theta - VI \cos(2\omega t - \theta)$$


we can write

$$p(t) = V [I \cos \theta (1 - \cos 2\omega t) + I \sin \theta \cdot \sin 2\omega t]$$

In the above equation we found two compts of current which are also marked in the phasor diagram.

$I \cos \theta$: current comp't in phase with voltage

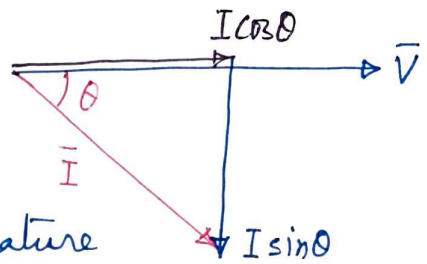$I \sin \theta$: current comp't in quadrature (at 90°) to voltage



The in phase comp't $I \cos \theta$ is actually feeding real power or active power (average) to the load given by

$$P_{avg} = P = VI \cos \theta \quad \text{where } V = \text{rms value of voltage} \\ I = \text{ " " " current}$$

$\cos \theta$ is defined as power factor.

Again the product of V & I is called apparent power (S).

$$\therefore S = VI$$

Thus the power factor is defined as

$$pf = \cos \theta = \frac{\text{Active power}}{\text{Apparent power}} = \frac{VI \cos \theta}{VI}$$

The unit of active power is watt/W but the unit of apparent power is Volt-Ampere (VA).


The quadrature comp't $I \sin \theta$ is responsible for another power which is known as reactive power, Q .

$$Q = VI \sin \theta$$

The unit of reactive power is volt-amp-reactive (VAR).

Reactive power will be taken as positive for lagging and negative for leading power factor load. The complex power phasor diagram is shown where

$$\bar{S} = P + jQ$$

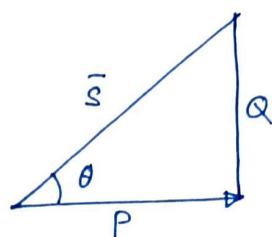

Complex power

It is convenient to express power in complex form.

$$\bar{S} = \bar{V} \bar{I}^* \quad \text{where } \bar{I}^* \text{ is the conjugate of } \bar{I}$$

$$\text{Let } \bar{V} = V \angle 0 = V e^{j0}$$

$$\bar{I} = I \angle -\theta = I e^{-j\theta} \quad (\because \bar{I} \text{ lags } \bar{V} \text{ by } \theta)$$

$$\therefore \bar{S} = \bar{V} \bar{I}^*$$

$$= V e^{j0} \cdot I e^{j\theta}$$

$$= VI e^{j\theta}$$

$$= VI (\cos \theta + j \sin \theta)$$

$$= VI \cos \theta + j VI \sin \theta$$

$$= P + jQ \quad [Q \text{ is +ve for lagging pf}]$$

$$S = \sqrt{P^2 + Q^2}$$

$$\text{and pf} = \cos \theta = \cos \left[\tan^{-1} \frac{Q}{P} \right] \quad ; \quad \begin{array}{l} \text{lagging for +ve } Q \\ \text{leading for -ve } Q. \end{array}$$

Consider an RL ckt where


$$\bar{S} = \bar{V} \bar{I}^*$$

$$= \bar{I} \bar{Z} \bar{I}^*$$

$$= \bar{Z} \bar{I}^2$$

$$= (R + jX_L) I^2$$

$$= RI^2 + jX_L I^2$$




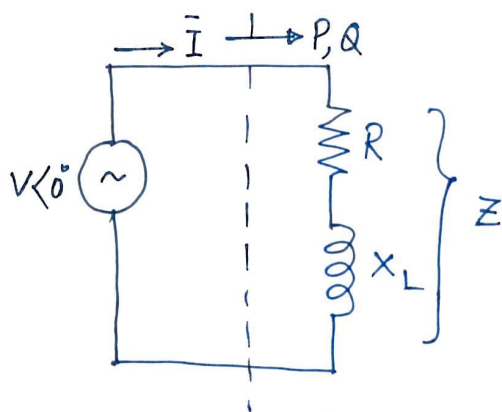


$$\therefore P = RI^2 = \text{real power consumed in resistive element}$$

$$Q = X_L I^2 = \text{reactive power consumed in reactive element (inductive)}$$

[Note: It is customary always to take Q as nonnegative. The -ve VAR is represented by VAR (capacitive)]

Power triangle

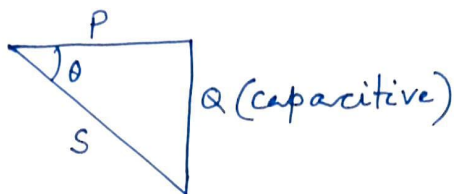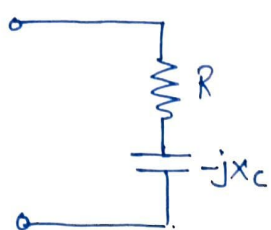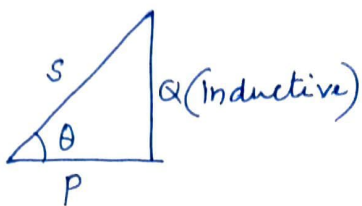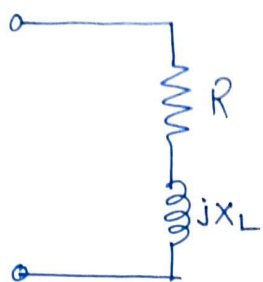

Ex. A certain passive network has equivalent impedance $\bar{Z} = 3 + j4 (\Omega)$ and an applied voltage $v(t) = 42.5 \cos(1000t + 30^\circ)$.
Give complete power information.

$$\bar{V} = V \angle \theta = \frac{42.5}{\sqrt{2}} \angle 30^\circ \text{ (V)}$$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{\left(\frac{42.5}{\sqrt{2}}\right) \angle 30^\circ}{3 + j4} = \frac{\left(\frac{42.5}{\sqrt{2}}\right) \angle 30^\circ}{5 \angle 53.13^\circ} = \frac{8.5}{\sqrt{2}} \angle -23.13^\circ \text{ (A)}$$


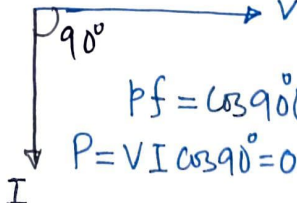
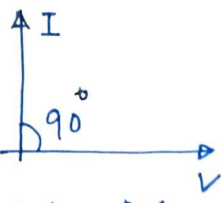
$$\begin{aligned} \bar{S} &= \bar{V} \bar{I}^* = \left(\frac{42.5}{\sqrt{2}} \angle 30^\circ\right) \left(\frac{8.5}{\sqrt{2}} \angle 23.13^\circ\right) \\ &= 180.6 \angle 53.13^\circ = 108.4 + j144.5 \\ &= P + jQ \end{aligned}$$

\therefore Active power, $P = 108.4 \text{ W}$,



Reactive power, $Q = 144.5 \text{ VAR}$, (inductive)

Apparent " $S = 180.6 \text{ VA}$

and power factor, $\text{pf} = \cos 53.13^\circ = 0.6$ (lagging)



Ex.	<u>Resistive ckt</u>	<u>Pure Inductive ckt</u>	<u>Pure Capacitive ckt</u>
	R	L	C
			
	$\text{pf} = \cos 0^\circ = 1$ (unity power factor)	$\text{pf} = \cos 90^\circ$ (lag)	$\text{pf} = \cos 90^\circ$ (lead)
	$P = VI \cos 0^\circ = VI$	$P = VI \cos 90^\circ = 0$	$P = VI \cos 90^\circ = 0$

Power factor improvement

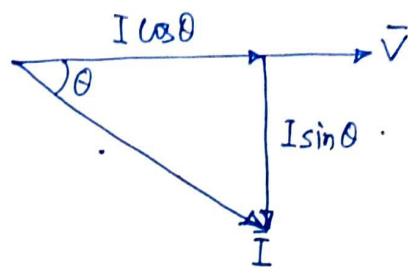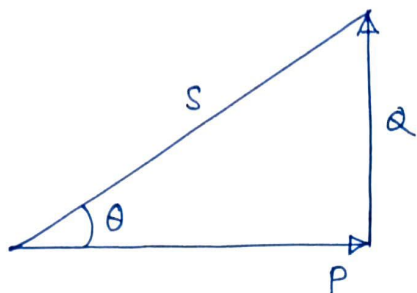

We can improve the pf by reducing Q .

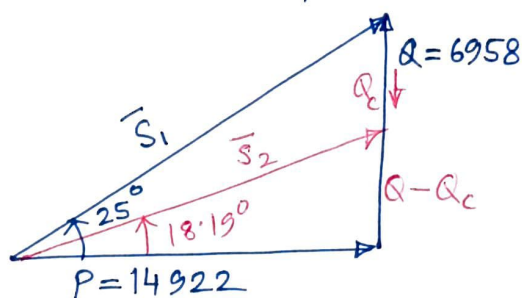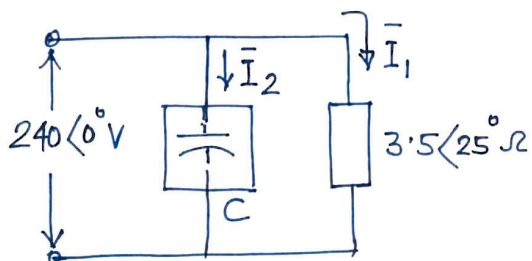Ex. How much capacitive Q must be provided by the capacitor bank in the circuit to improve the pf to 0.95 lagging?



Before capacitor bank is added, $pf = \cos 25^\circ = 0.906$ (lag)

$$\bar{I}_1 = \frac{240 \angle 0^\circ}{3.5 \angle 25^\circ} = 68.6 \angle -25^\circ \text{ (A)}$$

$$\bar{S}_1 = \bar{V} \bar{I}_1^* = (240 \angle 0^\circ) (68.6 \angle 25^\circ) = 16464 \angle 25^\circ = 14922 + j6958$$

After the improvement, the triangle has the same P , but its angle is $\cos^{-1}(0.95) = 18.19$

Let Q is reduced by Q_c

$$\therefore \tan 18.19 = \frac{Q - Q_c}{P} = \frac{6958 - Q_c}{14922}$$

$$\Rightarrow Q_c = 2054.8 \text{ VAR (capacitive)}$$

The new value of apparent power is

$$S_2 = \sqrt{P^2 + Q^2} = \sqrt{(14922)^2 + (4904)^2} = 15707.2 \text{ VA} \approx 15707 \text{ VA}$$

Total decrease in apparent power after improvement of power factor to 0.95 (lag) is 757 VA (around 4.6%)