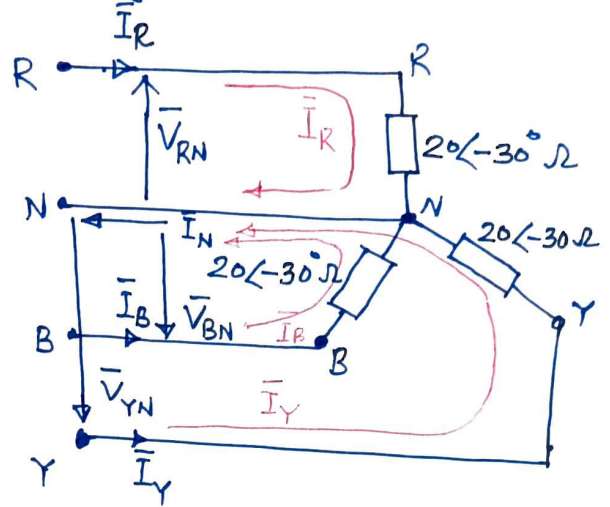


Ex. A 3- $\phi$ , 4 wire system with an effective line voltage of 120 V, has three impedances of  $20\angle -30^\circ \Omega$  in a Y-connection. Determine the line currents and draw the voltage-current phasor diagram.

$$\bar{Z} = 20\angle -30^\circ \Omega$$

$$\text{Line voltage, } V_L = 120 \text{ V}$$

$$\begin{aligned} \text{Phase voltage, } V_{ph} &= \frac{V_L}{\sqrt{3}} \quad (\text{for Y}) \\ &= \frac{120}{\sqrt{3}} \text{ V} \\ &= 69.28 \text{ V} \end{aligned}$$



Considering sequence RYB and phase voltages


$$\begin{aligned} \bar{V}_{RN} &= |\bar{V}_{RN}| \angle 0^\circ, \quad \bar{V}_{YN} = |\bar{V}_{YN}| \angle -120^\circ, \quad \bar{V}_{BN} = |\bar{V}_{BN}| \angle -240^\circ \\ &= V_{ph} \angle 0^\circ, \quad = V_{ph} \angle -120^\circ, \quad = V_{ph} \angle -240^\circ \end{aligned}$$

Phase currents = Line currents (in case of Y)

$$\therefore \bar{I}_R = \frac{\bar{V}_{RN}}{\bar{Z}} = \frac{V_{ph} \angle 0^\circ}{20 \angle -30^\circ} = 3.464 \angle 30^\circ \text{ A}$$

$$\bar{I}_Y = \frac{\bar{V}_{YN}}{\bar{Z}} = \frac{V_{ph} \angle -120^\circ}{20 \angle -30^\circ} = 3.464 \angle -90^\circ \text{ A}$$
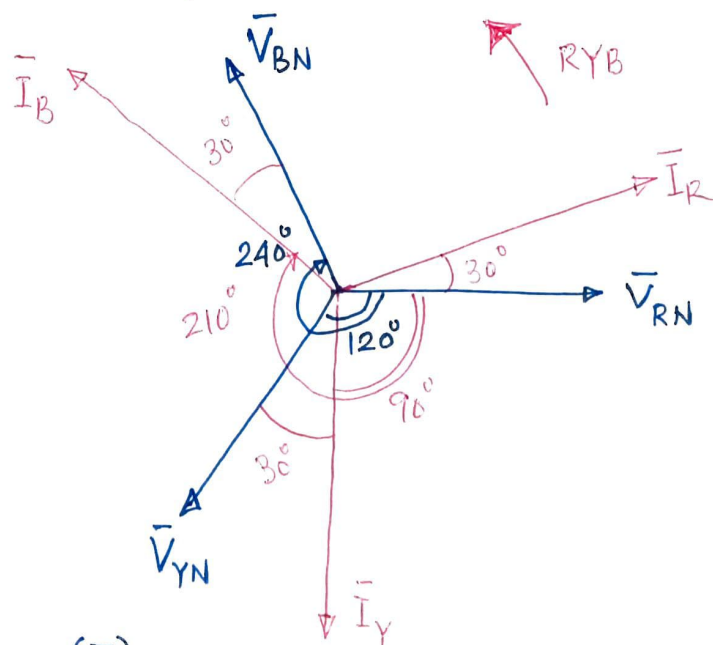
$$\bar{I}_B = \frac{\bar{V}_{BN}}{\bar{Z}} = \frac{V_{ph} \angle -240^\circ}{20 \angle -30^\circ} = 3.464 \angle -210^\circ \text{ A}$$




Ex A 3- $\phi$ , ~~3~~ system, with an effective voltage 70.7V, has a balanced  $\Delta$ -connected load with impedance  $20\angle 45^\circ \Omega$ . Obtain the line currents and draw the voltage-current phasor diagram.

$$V_L = V_{ph} \text{ (in } \Delta \text{)}$$

$$= 70.7V$$

$$\bar{Z} = 20\angle 45^\circ \Omega$$

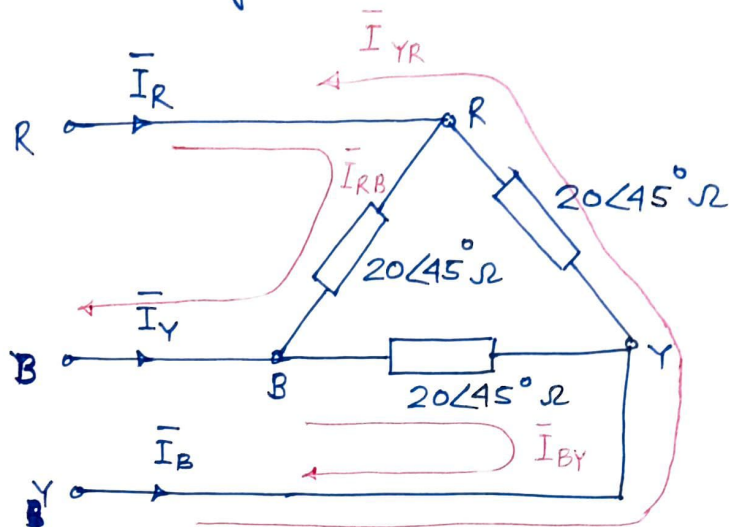

Phase voltages :-  $\bar{V}_{RY} = |\bar{V}_{RY}|\angle 0^\circ$ ,  $\bar{V}_{YB} = |\bar{V}_{YB}|\angle -120^\circ$   
 $\bar{V}_{BR} = |\bar{V}_{BR}|\angle -240^\circ$ ,  $|\bar{V}_{RY}| = |\bar{V}_{YB}| = |\bar{V}_{BR}| = 70.7V$

$$\bar{I}_{RY} = \frac{70.7\angle 0^\circ}{20\angle 45^\circ} = 3.535\angle -45^\circ \text{ A}, \quad \bar{I}_{YB} = \frac{70.7\angle -120^\circ}{20\angle 45^\circ} = 3.535\angle -165^\circ \text{ (A)}$$

$$\bar{I}_{BR} = \frac{70.7\angle -240^\circ}{20\angle 45^\circ} = 3.535\angle -285^\circ = 3.535\angle 75^\circ \text{ (A)}$$


$$\bar{I}_R = \bar{I}_{RB} + \bar{I}_{RY} = -\bar{I}_{BR} + \bar{I}_{RY}$$

Ex A 3- $\phi$  power system with a line voltage of 400 V is supplying a  $\Delta$ -connected load of 1500 W at 0.8 power factor lagging. Determine the phase and line currents and also the phase impedance.

$$V_L = 400 \text{ V}$$

$$V_p = V_L = 400 \text{ V}$$

( $\Delta$ -connected)

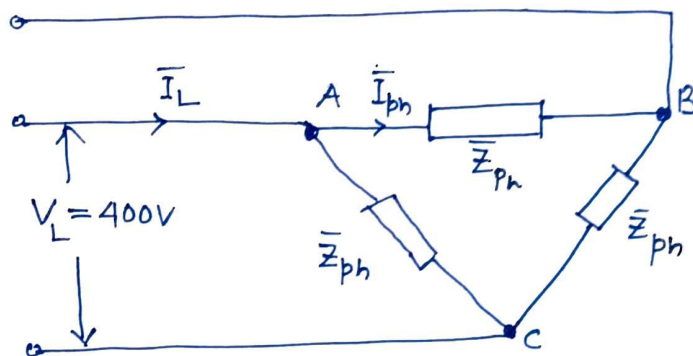

Power,  $P = \sqrt{3} V_L I_L \cos \theta$

$$\Rightarrow 1500 = \sqrt{3} \times 400 \times I_L \times 0.8$$

$$\Rightarrow I_L = \frac{1500}{\sqrt{3} \times 400 \times 0.8} = 2.71 \text{ A}$$

In  $\Delta$ -connected system  $I_L = \sqrt{3} I_{ph} \quad \therefore I_{ph} = 1.56 \text{ A}$

Since the pf is 0.8 lagging,  $\cos \theta = 0.8 \Rightarrow \theta = 36.9^\circ$

$$\therefore \bar{I}_{ph} = 1.56 \angle -36.9^\circ$$

$$\therefore \bar{Z}_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400 \angle 0^\circ}{1.56 \angle -36.9^\circ} = 256 \angle 36.9^\circ (\Omega) //$$

Ex A balanced  $\Delta$ -connected load of impedance  $16 + j12 \Omega$ /phase is connected to a 3- $\phi$  400V supply.


Find the phase current, line current, power factor, power, reactive VA and total VA. Also draw a phasor diagram.

[Ans.  $\bar{I}_{ph} = 20 \angle -36.9^\circ \text{ A}$ , pf = 0.8 (lag),  $P = 19.2 \text{ kW}$ ,

$Q = 14.4 \text{ kVAR}$ ,  $S = 24 \text{ kVA}$ ]

Ex A balanced star-connected load is supplied from a symmetrical 3- $\phi$ , 400V (line-to-line) supply. The current in each phase is 50A and lags  $30^\circ$  behind the phase voltage. Find (a) phase voltage (b) phase impedance and (c) active power drawn by the load. Also draw the phasor diagram.

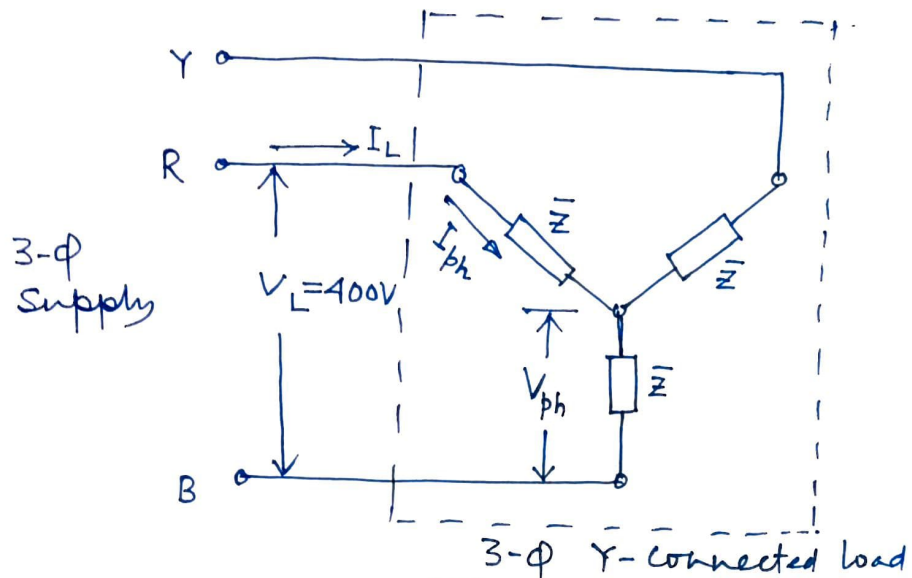[Ans. (a) 231 V (b)  $4 + j2.31 \Omega$  (c) 30 kW.]



~~V\_L = 400V~~  $V_L = \sqrt{3} V_{ph}$   $V_{ph} = \frac{400}{\sqrt{3}} = 231 \text{ V (reference phasor)}$

$\bar{I}_L = \bar{I}_{ph} = 50 \text{ A and lags } 30^\circ = 50 \angle -30^\circ \text{ A}$

$\therefore \bar{Z} = \frac{\bar{V}_{ph}}{\bar{I}_{ph}} = \frac{231 \angle 0^\circ}{50 \angle -30^\circ} =$

$P = \sqrt{3} V_L I_L \cos \theta$   
 $= \sqrt{3} \times 400 \times 50 \cos 30^\circ$

