

SINUSOIDAL STEADY-STATE ANALYSIS

When sinusoidal excitation is applied to a circuit, the response has two parts:

- (i) Natural response or Transient response
- (ii) steady-state response (forced response)

At this stage, we are not interested to transient response.

If we apply a sinusoidal voltage in a circuit (linear)

then the steady-state response $i(t)$ has the same frequency

with the voltage but with some changes in phase.

Let $v(t) = V_m \sin \omega t$ then

$$i(t) = I_m \sin(\omega t \pm \phi)$$

There are three basic electrical circuit elements:

Resistance, Inductance and Capacitance. Let us establish voltage-current relationships of all these three elements.




1. Resistance (R)

$$v(t) = V_m \sin \omega t$$

$$i(t) = \frac{v(t)}{R}$$

$$= \frac{V_m}{R} \sin \omega t$$
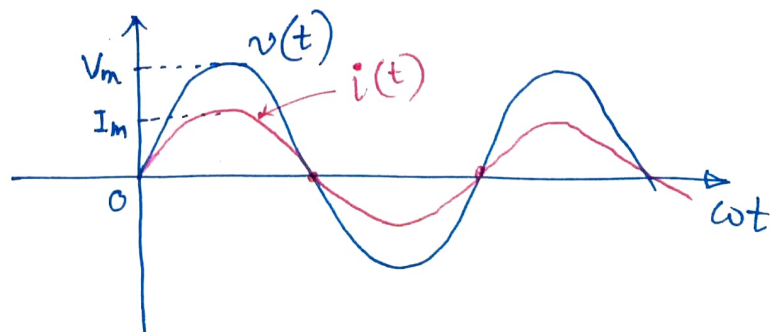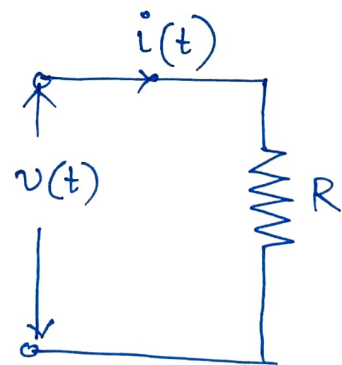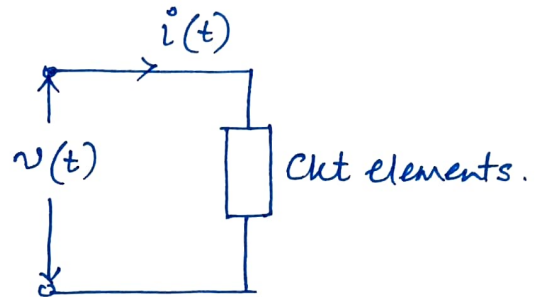
$$= I_m \sin \omega t \quad \text{where } I_m = \frac{V_m}{R}$$



In phasor notation

$$\bar{V} = V \angle 0^\circ$$

R: scalar

V = RMS value.

$$\bar{I} = \frac{V \angle 0^\circ}{R}$$


$$= \frac{V}{R} \angle 0^\circ = I_m \angle 0^\circ$$



So the phase difference between voltage and current is zero, i.e. both voltage and current are in phase.

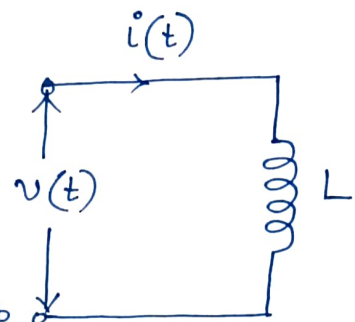2. Inductance (L)

In case of inductance L, the voltage-current relationship is given by $v_L(t) = L \frac{di(t)}{dt}$.



Let us assume that $i(t) = I_m \sin \omega t$

$$\begin{aligned} \therefore v_L(t) = v(t) &= L \frac{d}{dt} (I_m \sin \omega t) \\ &= \omega L I_m \cos \omega t \\ &= \omega L I_m \sin(\omega t + 90^\circ) \\ &= V_m \sin(\omega t + 90^\circ) \end{aligned}$$



Where $V_m = \omega L I_m$

$$\begin{aligned} \Rightarrow \frac{V_m}{I_m} &= \omega L = \text{inductive reactance} \\ &= X_L (\Omega) \end{aligned}$$

In phasor notation

$$\bar{I} = I \angle 0^\circ$$
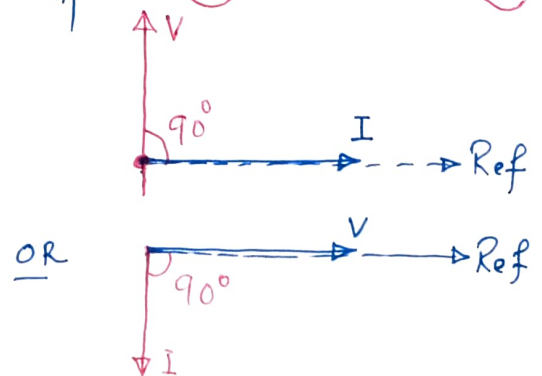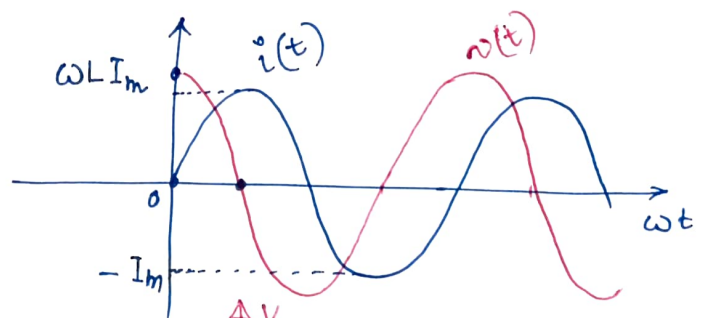
$$\begin{aligned} \bar{V} &= \bar{V} \angle 90^\circ = \sqrt{2} \omega L I_m \angle 90^\circ \\ &= \sqrt{2} V_m \angle 90^\circ \end{aligned}$$



In case of inductance, the current is lagging behind the voltage by 90° .

In complex notation if $\bar{I} = I \angle 0^\circ$ then $\bar{V} = V \angle 90^\circ = jV$

$$\therefore \frac{\bar{V}}{\bar{I}} = \frac{V \angle 90^\circ}{I \angle 0^\circ} = \frac{jV}{I} = \frac{j\sqrt{2}\omega L I_m}{\sqrt{2}I_m} = j\omega L = jX_L$$

$X_L = 2\pi fL$ where f : frequency in Hz.

3. Capacitance

Let $v(t) = V_m \sin \omega t$

$$\therefore i(t) = C \cdot \frac{dv(t)}{dt}$$

$$= C \cdot \frac{d}{dt} [V_m \sin \omega t]$$




$$= C \cdot V_m \omega \cos \omega t$$

$$= \omega C V_m \sin(\omega t + 90^\circ)$$

$$= I_m \sin(\omega t + 90^\circ)$$

where $I_m = \omega C V_m$
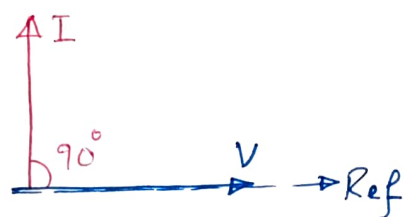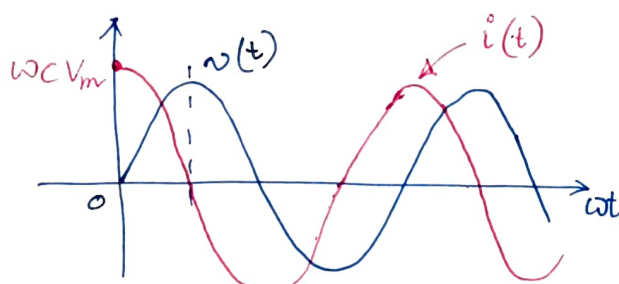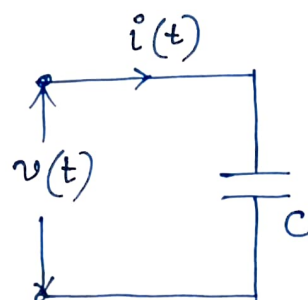
$$\Rightarrow \frac{V_m}{I_m} = \frac{1}{\omega C} = \text{capacitive reactance} = X_C$$



In phasor notation

$$\bar{V} = V \angle 0^\circ$$

$$\bar{I} = I \angle 90^\circ = \sqrt{2} \omega C I_m \angle 90^\circ = \sqrt{2} I_m \angle 90^\circ = jI$$

In case of capacitance, the current is leading the voltage by 90°

In complex notation, if $\bar{V} = V \angle 0^\circ$ then $\bar{I} = I \angle 90^\circ = jI$

$$\therefore \frac{\bar{V}}{\bar{I}} = \frac{V \angle 0^\circ}{I \angle 90^\circ} = \frac{V}{jI} = \frac{\sqrt{2}V_m}{j\sqrt{2}\omega C V_m} = \frac{1}{j\omega C} = \frac{1}{jX_C} = -jX_C$$

In summary,

R : voltage and current both are in phase

L : current is lagging behind voltage by 90°

C : current is leading the voltage by 90°

$X_L = \omega L = 2\pi fL = \text{inductive reactance}(\Omega)$

$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \text{capacitive reactance}(\Omega)$

In complex notation,

Inductive reactance $= jX_L = j\omega L$

Capacitive " $= -jX_C = -j\frac{1}{\omega C}$

Electrical ckt

1. RL ckt

$$\bar{V} = \bar{V}_R + \bar{V}_L$$

$$= \bar{I}R + \bar{I}X_L$$

$$= \bar{I}R + j\omega L \bar{I}$$

$$= (R + j\omega L) \bar{I}$$


$$= \bar{Z} \bar{I} \quad \text{where } \bar{Z} = R + j\omega L = \text{impedance of the ckt}$$

In polar form, $\bar{Z} = Z \angle \theta$

$$\text{where } Z = |\bar{Z}| = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + (\omega L)^2}$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Impedance triangle

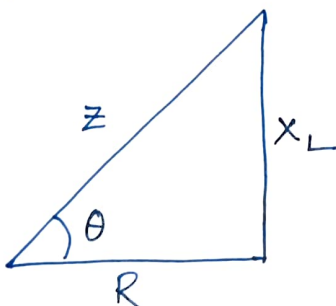

It must be observed that impedance is a complex number and not a phasor.

We have seen that $\bar{I} = \frac{\bar{V}}{\bar{Z}}$

Here $\bar{I} = \frac{\bar{V}}{\bar{Z}} = \bar{Y} \bar{V}$ where $\bar{Y} = \frac{1}{\bar{Z}} = \text{admittance (Y)}$

$$\therefore \bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{R + jX_L} = \frac{R}{R^2 + X_L^2} - j \frac{X_L}{R^2 + X_L^2}$$

$$= G - jB$$

where $G = \text{conductance}$ and $B = \text{susceptance}$

2. RC ckt

$$\bar{V} = \bar{V}_R + \bar{V}_C$$


$$= \bar{I}R + \bar{I}\bar{X}_C$$

$$= (R - jX_C) \bar{I}$$

$$= \bar{Z} \bar{I} \quad \text{where } \bar{Z} = R - jX_C = \text{impedance of the ckt}$$

$$|\bar{Z}| = \sqrt{R^2 + X_C^2}, \quad \theta = \tan^{-1} \left(\frac{-X_C}{R} \right) = -\tan^{-1} \frac{X_C}{R}$$
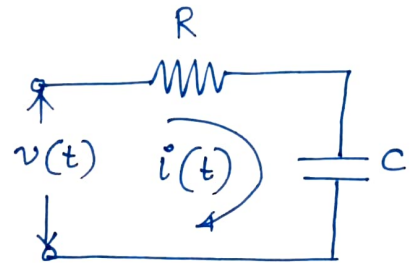
$$\therefore \bar{Z} = Z \angle -\tan^{-1} \left(\frac{X_C}{R} \right)$$



3. RLC series ckt


In phasor notation

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$= \bar{I}R + (jX_L) \bar{I} - (jX_C) \bar{I}$$

$$= [R + j(X_L - X_C)] \bar{I}$$

(assume that $X_L > X_C$)

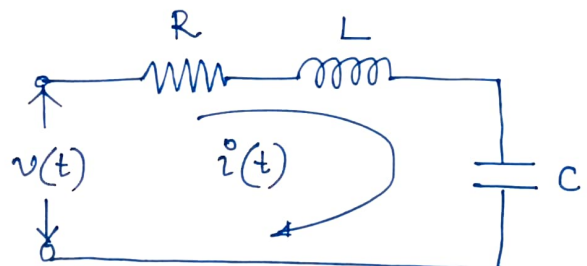


$$\therefore \text{Impedance, } \bar{Z} = R + j(X_L - X_C)$$

$$Z = |\bar{Z}| = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + X^2}$$


$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

Impedance triangle

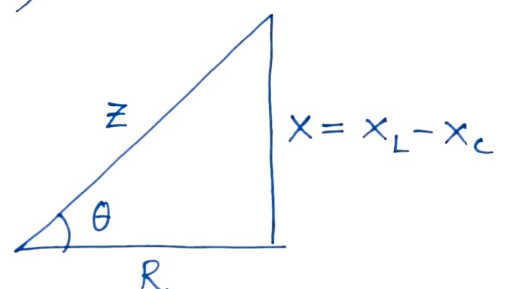


Phasor diagram


1. RL ckt

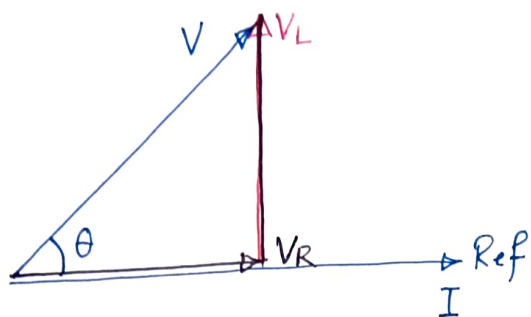


2. RC ckt

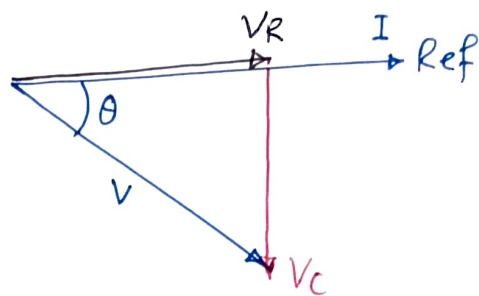

3. RLC ckt


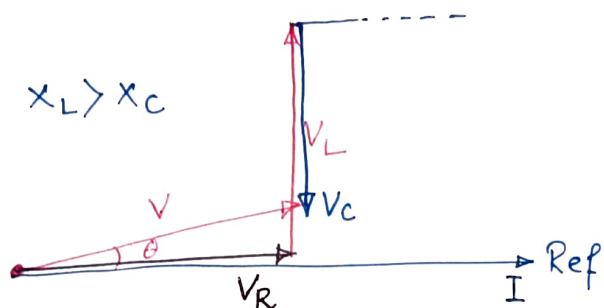


(Ckt is dominated by inductance)

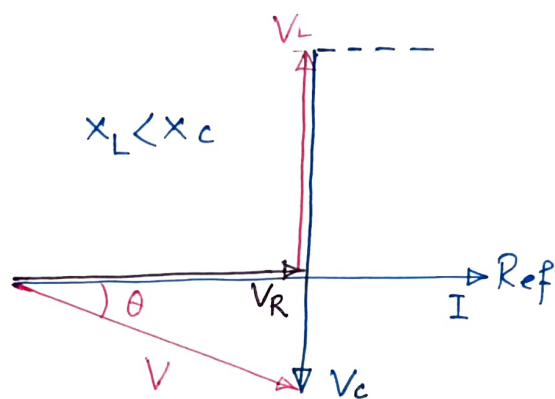

(Ckt is dominated by capacitance)

Alternative phasor diagram for RLC ckt

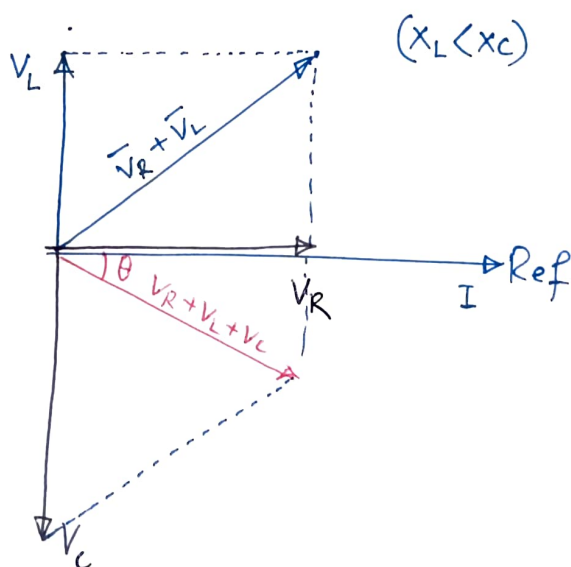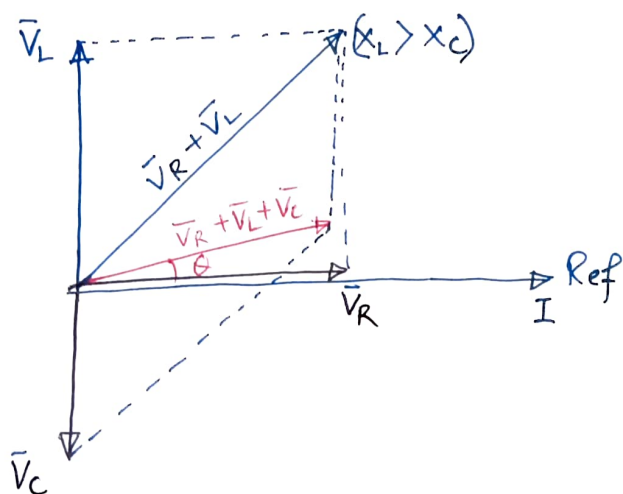

Ex


$$i(t) = 2 \sin 500t$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{10^2 + (2\pi fL)^2}$$

$$= \sqrt{10^2 + (\omega L)^2}$$
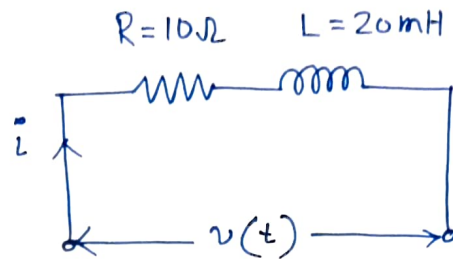
$$= \sqrt{100 + (500 \times 20 \times 10^{-3})^2} = 14.14$$



$$\theta = \tan^{-1} \frac{\omega L}{R}$$

$$= \tan^{-1} \left(\frac{500 \times 20 \times 10^{-3}}{10} \right) = 45^\circ$$


V = rms value of voltage, I = rms value of current

$$\therefore V = ZI = 14.14 \times \frac{2}{\sqrt{2}} = 20V \quad [\because I_m = 2]$$

$$\therefore v(t) = V_m \sin(\omega t + \phi)$$

$$= 20 \times \sqrt{2} \sin(500t + 45^\circ)$$

$$= 28.3 \sin(500t + 45^\circ) //$$

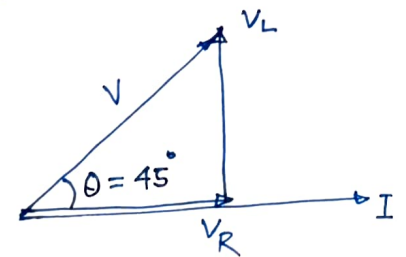


In complex notation

$$\bar{I} = 2\sqrt{2} \angle 0^\circ, \quad \bar{Z} = R + jX_L = 10 + j(500 \times 20 \times 10^{-3})$$
$$= 10 + j10$$

$$\bar{V} = \bar{I} \bar{Z} = (2\sqrt{2} \angle 0^\circ)(14.14 \angle 45^\circ) = 14.14 \angle 45^\circ$$
$$= 20 \angle 45^\circ$$


In sinusoidal waveform.
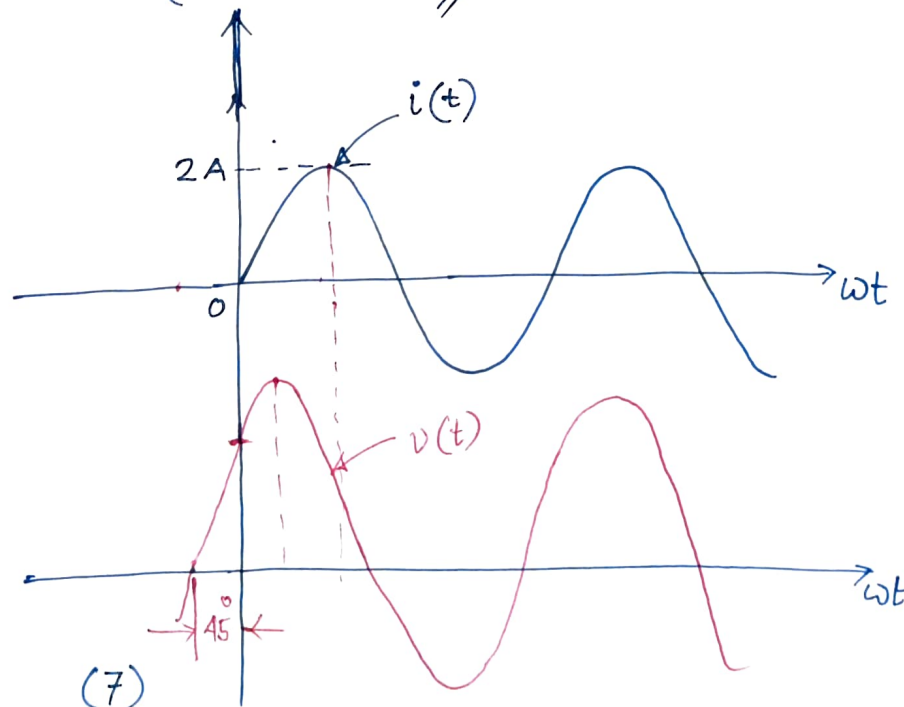
$$v(t) = \sqrt{2} V \sin(500t + 45^\circ)$$
$$= 28.3 \sin(500t + 45^\circ) //$$




(7)

Ex

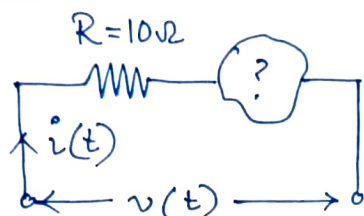

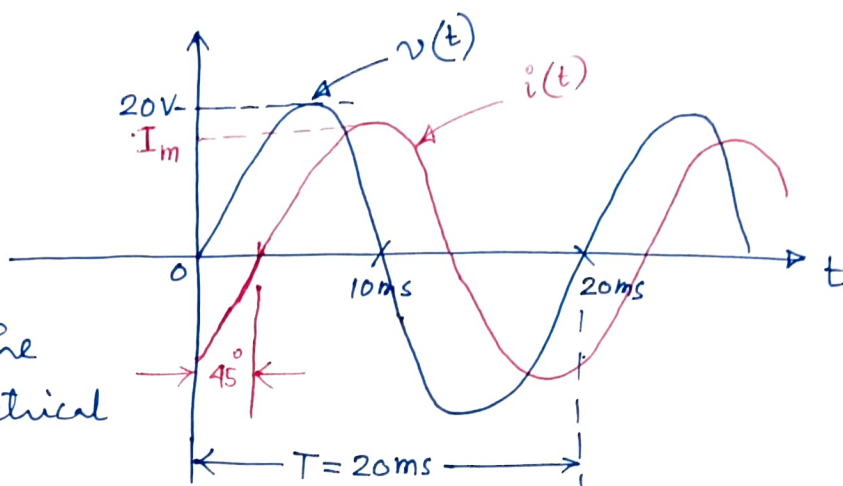Calculate I_m and the value of unknown electrical element.



Ex Find the two elements in a series ckt, given that the current and total voltage are

$$i(t) = 10 \cos(5000t - 23.13^\circ), \quad v(t) = 50 \cos(5000t + 30^\circ)$$

[Ans. $R = 3\Omega$, $L = 0.8 \text{ mH}$]

Ex A series ckt with $R = 2\Omega$ and $C = 200\mu F$, has a sinusoidal applied voltage with a frequency of 99.47 MHz . If the max. voltage across the capacitance is $24V$, what is the max. voltage across the series combination?

Ex Obtain the sum of the three voltages

$$v_1(t) = 147.3 \cos(\omega t + 98.1^\circ) \text{ (V)} \quad v_2(t) = 294.6 \cos(\omega t - 45^\circ)$$

and $v_3(t) = 88.4 \sin(\omega t + 135^\circ)$

Ex. An RLC series ckt has a current which lags the applied voltage by 30° . The inductor voltage maximum is twice the capacitor voltage maximum, and $v_L = 10 \sin 1000t \text{ (V)}$. Determine L and C , given that $R = 20\Omega$

[Ans. $L = 23.1 \text{ mH}$, $C = 86.5 \mu F$]

Series-parallel combination of R-L-C ckt

Impedance in series: $\bar{Z} = \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 + \dots$

Impedance in parallel: $\frac{1}{\bar{Z}} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3} + \dots$

Admittance in series: $\bar{Y} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 + \dots$

Admittance in parallel: $\frac{1}{\bar{Y}} = \frac{1}{\bar{Y}_1} + \frac{1}{\bar{Y}_2} + \dots$

For series combination $\bar{Z} = \bar{Z}_1 + \bar{Z}_2 + \bar{Z}_3 + \dots$ is convenient

For parallel " $\frac{1}{\bar{Z}} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2} + \frac{1}{\bar{Z}_3} + \dots$

$\Rightarrow \bar{Y} = \bar{Y}_1 + \bar{Y}_2 + \bar{Y}_3 + \dots$ is convenient.


1. R-L parallel ckt

$$\bar{Z}_{eq} = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$$


$$\bar{I} = \frac{\bar{V}}{\bar{Z}_{eq}} = \bar{Y}_{eq} \bar{V}$$

$$= (\bar{Y}_1 + \bar{Y}_2) \bar{V}$$
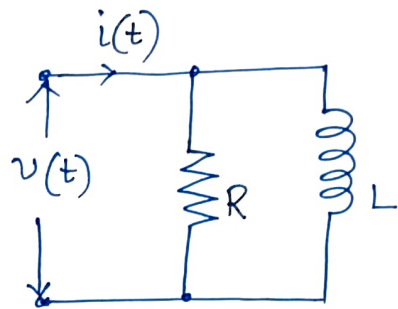
$$\bar{Y}_1 = \frac{1}{\bar{Z}_1}, \quad \bar{Y}_2 = \frac{1}{\bar{Z}_2}$$



OR

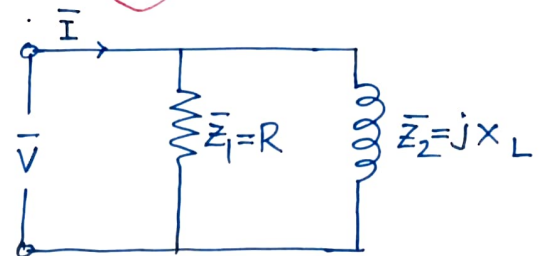


2. R-C parallel ckt


$$\bar{Z}_{eq} = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2}$$

$$\bar{Z}_1 = R \Rightarrow \bar{Y}_1 = \frac{1}{R} = G$$
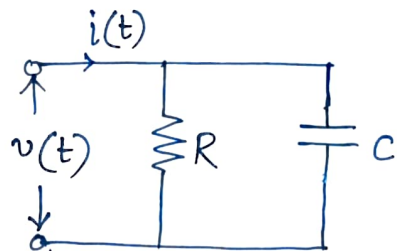
$$\bar{Z}_2 = -jX_C \Rightarrow \bar{Y}_2 = \frac{1}{-jX_C} = +jB$$



OR

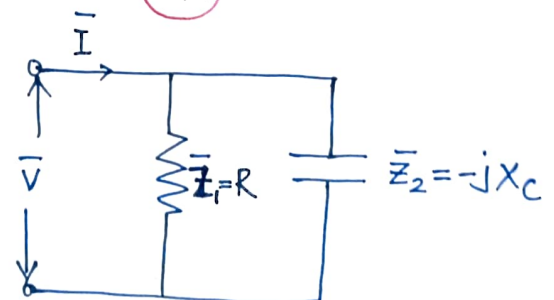

3. R-L-C parallel circuit

$$\bar{Z}_1 = R_1 + jX_L \Rightarrow \bar{Y}_1 = \frac{1}{\bar{Z}_1} = G_1 - jB_1$$

$$\bar{Z}_2 = R_2 - jX_C \Rightarrow \bar{Y}_2 = \frac{1}{\bar{Z}_2} = G_2 + jB_2$$

$$\bar{Y}_{eq} = \bar{Y}_1 + \bar{Y}_2 = (G_1 + G_2) + j(B_2 - B_1)$$


=

$$\bar{I} = \bar{Y}_{eq} \bar{V}$$


$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

$$\bar{I}_1 = \bar{V} \bar{Y}_1, \quad \bar{I}_2 = \bar{V} \bar{Y}_2$$

$B_2 > B_1$

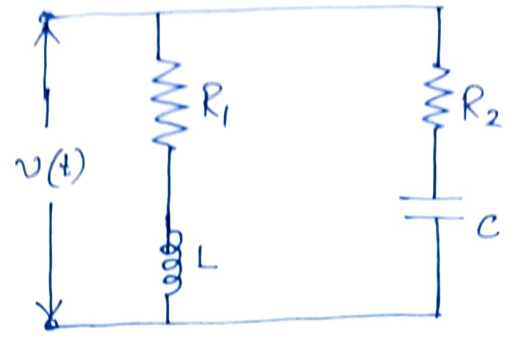

OR

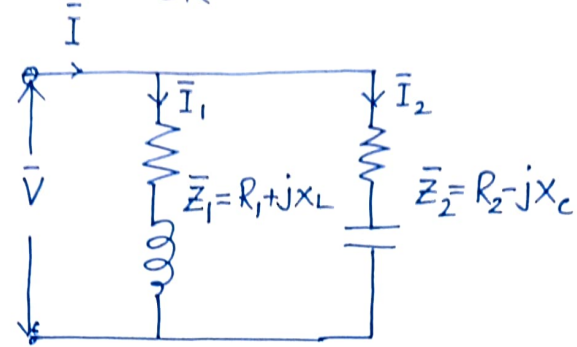


Ex Obtain \bar{Z}_{eq} and \bar{Y}_{eq} for the circuit of Fig.

$$\bar{Z}_1 = 10 + j20 = 22.4 \angle 63.43^\circ$$

$$\bar{Z}_2 = 15 - j15 = 21.2 \angle -45^\circ$$

$$\bar{Z}_{eq} = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} = \frac{(22.4 \angle 63.43^\circ)(21.2 \angle -45^\circ)}{(10 + j20) + (15 - j15)}$$

$$= 18.63 \angle -7.12^\circ \Omega$$

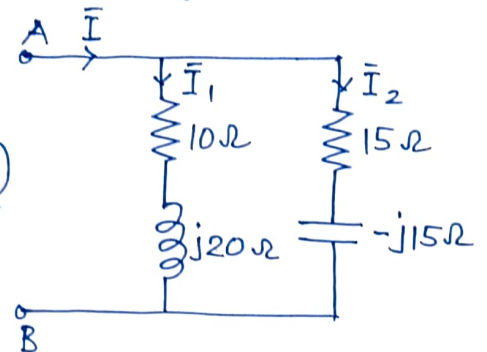

$$\bar{Y}_{eq} = \frac{1}{\bar{Z}_{eq}} = 0.0537 \angle -7.12^\circ \text{ (u) OR (S)}$$

mho siemens

If $\bar{V} = 60 \angle 0^\circ$ is applied across AB find $\bar{I}, \bar{I}_1, \bar{I}_2$

